

The data path and the controller are very similar to the midterm project, but few things have been changed:


- Instead of 1 kernel, now we have many kernels, in the source code, the parameter `'nkernel'` is used to define number of kernels.
- Number of clocks to read kernels is expanded from 4 to $4 \times \text{nkernel}$.
- A `'counter_nkernel'`, is added to the controller to show in which kernel we should load the memory.
- The addresses of kernels are considered to be ranged from `'y'` to `'4 × nkernel + y'`, all kernels are expected to be continuously after each other in the memory.
- Number of MACs expanded to `'nkernel'`.
- The output of i-th MAC will be saved on i-th OFM (output memory) respectively.
- `'z'` is equal for all OFMs.
- `'generate'` method is used for instancing multiple modules.

And the most important thing:

- All calculations are in parallel and at the same time.

The diagrams can be seen in the following pages.

Controller:

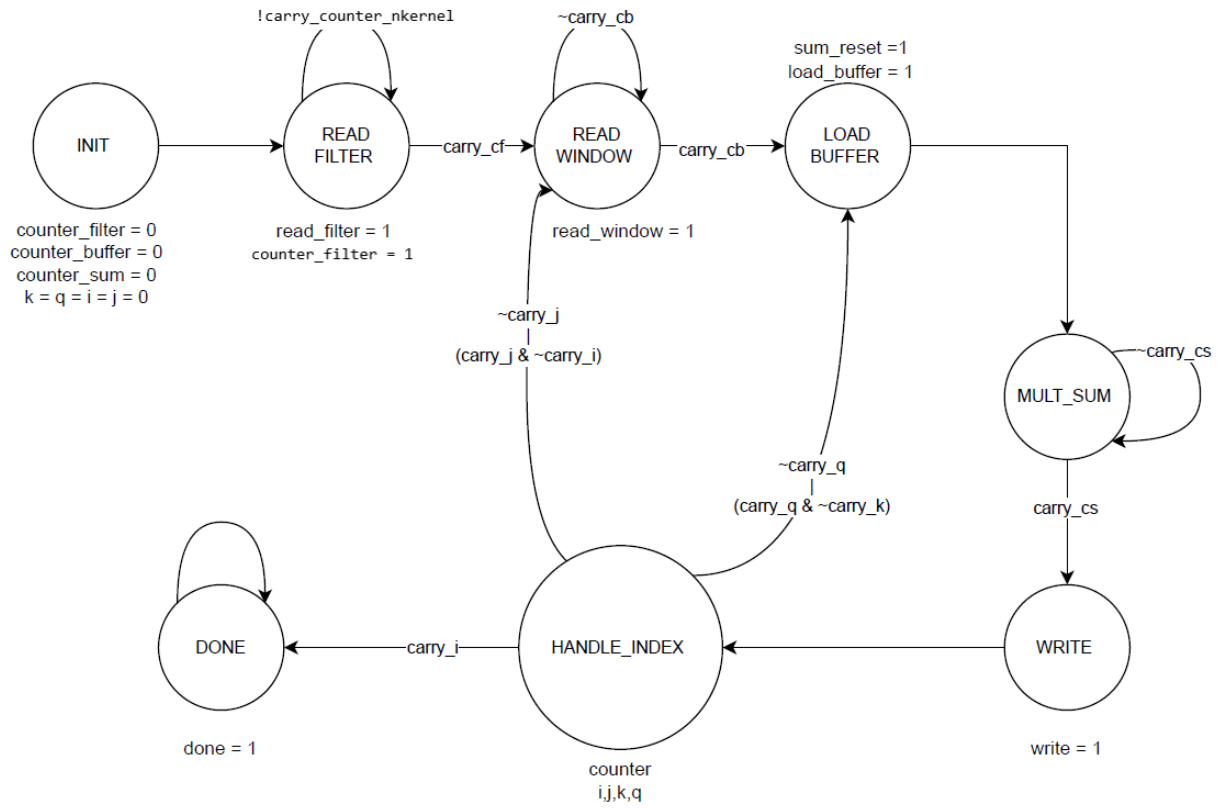

Datapath:

