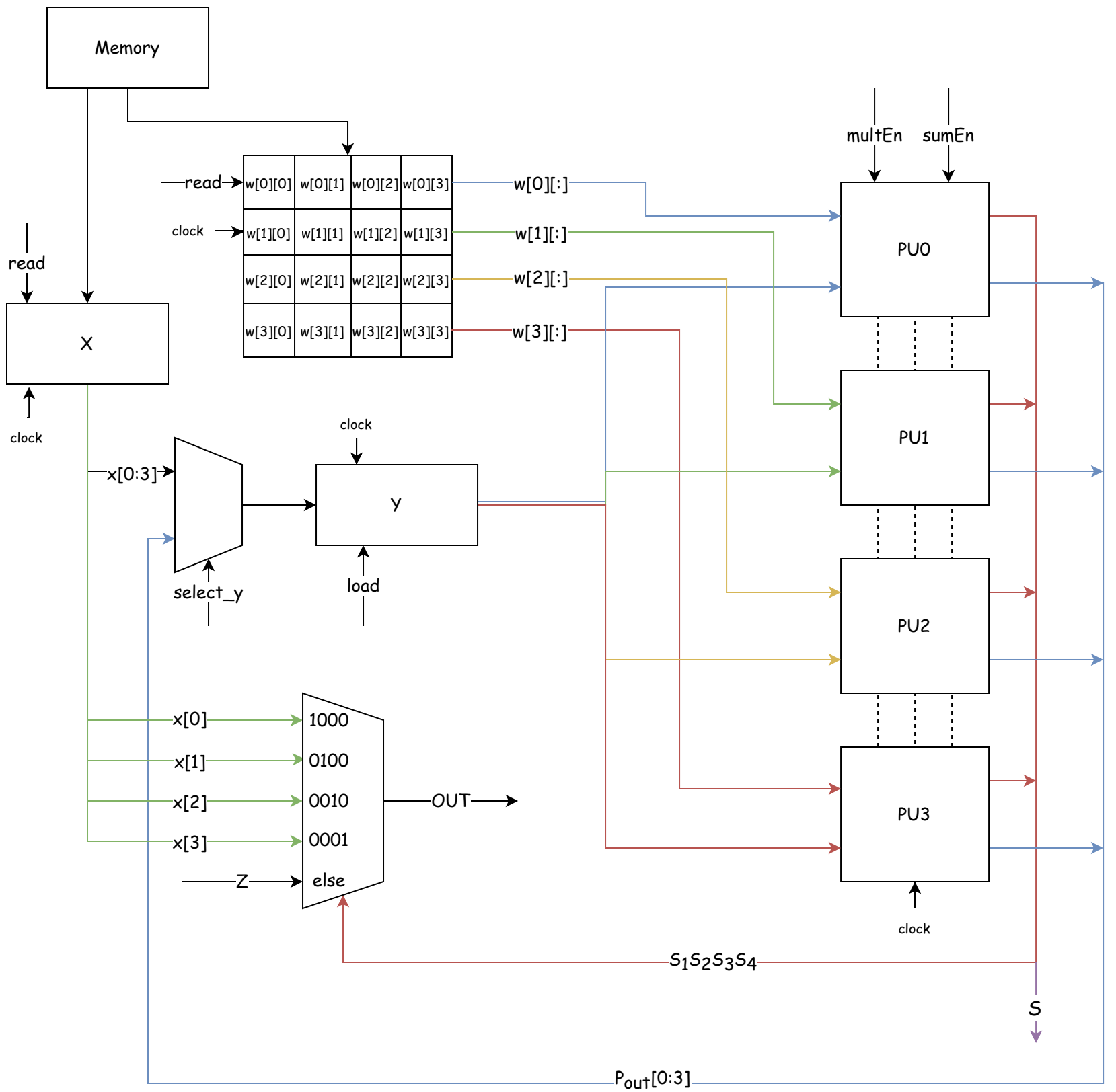


- To make sure the output of a PU(process unit) is ready in proper time, we added 2 register and expand PU execution time to three clocks:
 1. Multiplication
 2. Adder tree
 3. Activation + Load
- An X register is added to have original value of neurons for whenever it be needed.
- Arithmetic operations will be performed using the Y register.
- Select of output MUX is a 4 bit one-hot.
- Output is maximum value of neurons.

The datapath and controller diagrams can be found on the following pages:



$$S = S_1 \sim S_2 \sim S_3 \sim S_4 + \sim S_1 S_2 \sim S_3 \sim S_4 + \sim S_1 \sim S_2 S_3 \sim S_4 + \sim S_1 \sim S_2 \sim S_3 S_4$$

