 
 
 


**Module C1:**



	XOR	AND	OR	NOT
A0	0	0	A	1
A1	1	0	1	1
SA	B	0	B	1
B0	1	0	1	0
B1	0	A	1	0
SB	B	B	1	0
S0	A	C	C	A
S1	0	0	0	0

*Module C2:*

	MUX2	MUX4
D00	A	A
D01	B	B
D10	-	C
D11	-	D
A1	0	Select[1]
B1	0	0
A0	Select	Select[0]
B0	1	1


**Module S2:**

	reg
D00	Out
D01	In
D10	-
D11	-
A0	0
A1	0
B0	Enable
B1	Out

  
**Full Adder:****Bit Multiplier:**

- To implement Adder and Multiplier, we just cascaded the Full adder and bit multiplier respectively.

*2's complement:*

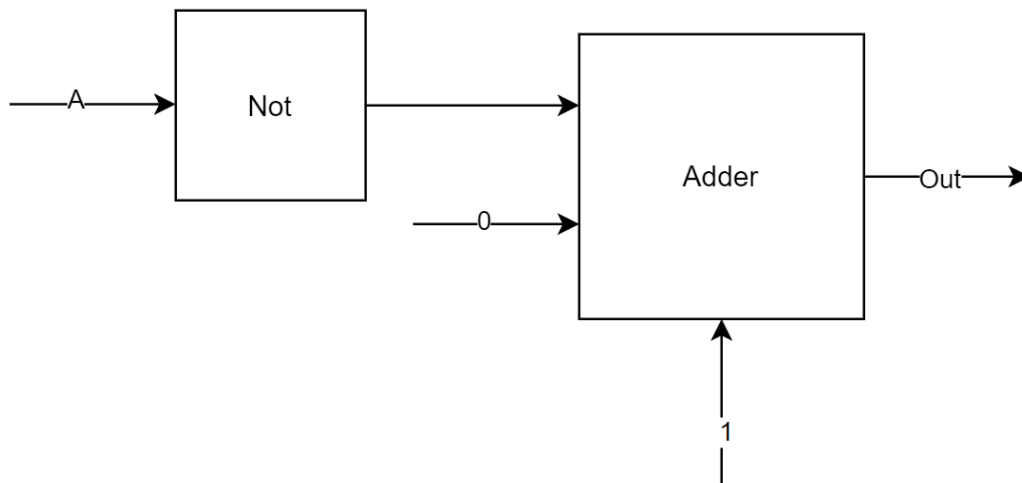


*Absolute:*

 


To do multiplication:

- First we multiply absolute of 2 numbers.
- Then according to bit sign, it may be needed to complement result.

*One-Hot multiplexer:*

 

### Comparator:

 

### Arithmetic:

- Numbers are 5-bit fixed-point floats. 1 sign bit, 1 integer bit and 3 fractional bits.

### Datapath:

- Same as previous CA, the design is attached to 'doc'.
- 'W' and 'X' which are weights and layer inputs respectively will be read from file to increase flexibility.

### Controller:

- Controller logic is same as previous CA, but to re-implement using ACT modules, we used these modules:
  - Register
  - Comparator
  - One-Hot Multiplexer

Where all implementations are mentioned before.

- The diagram can be found in the next page.

